
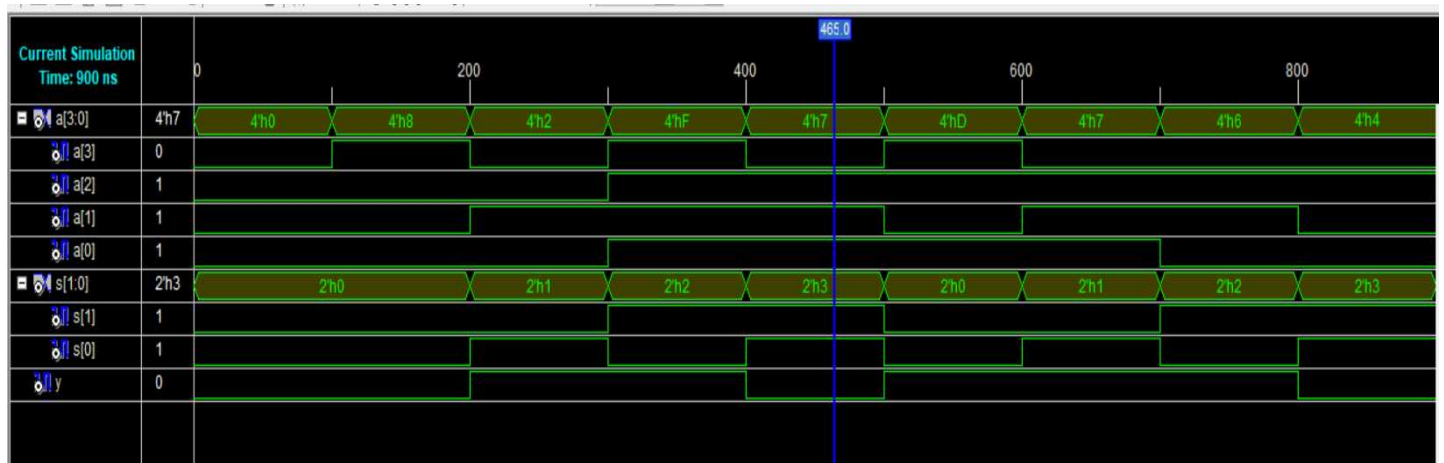



4 X 1 Multiplexer – Structural Model

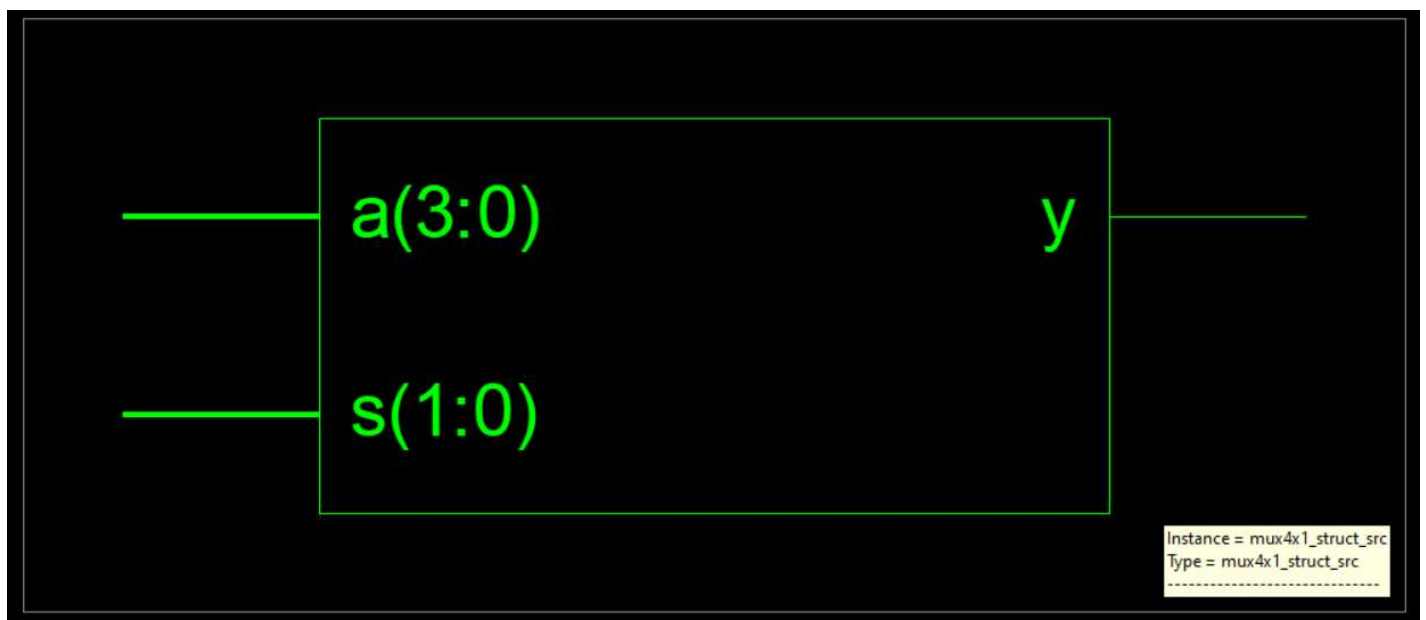


Waveform




RTL Schematic

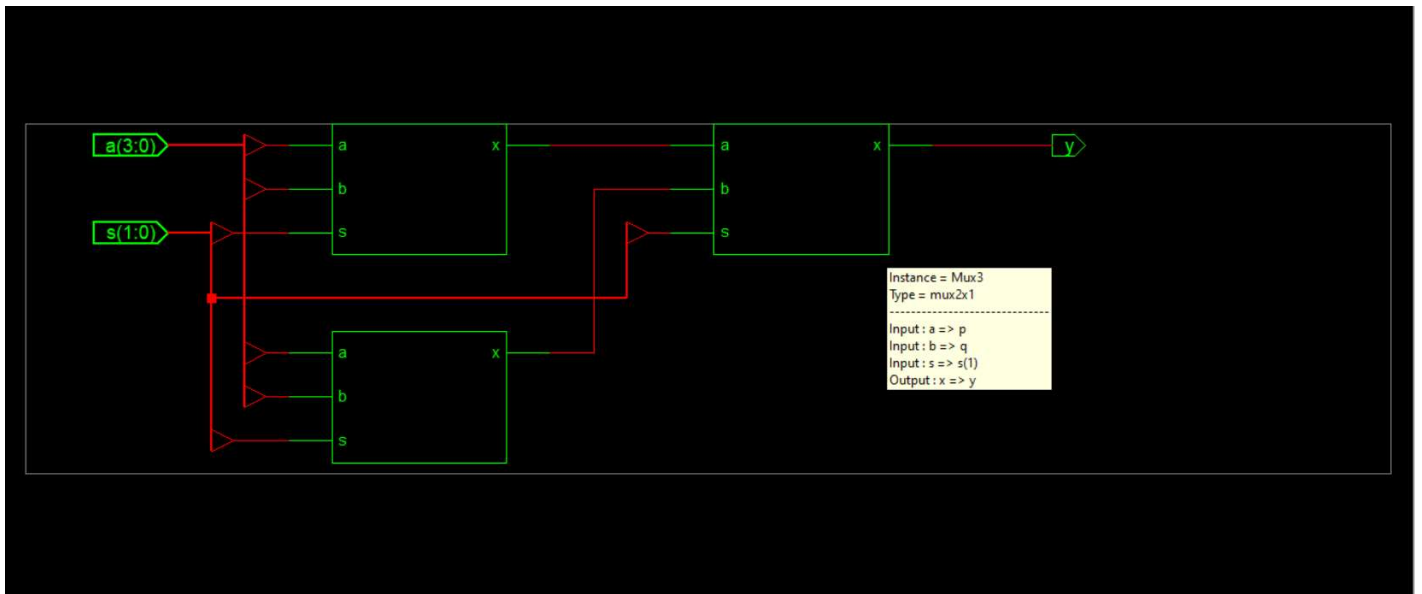

Detailed RTL Schematic Circuit

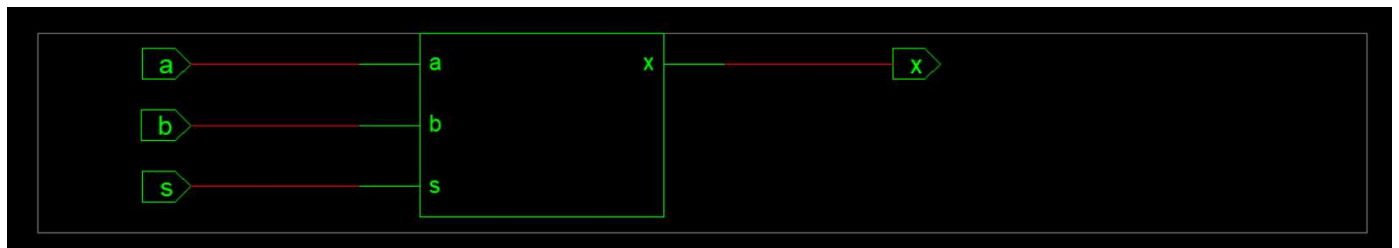

RTL Schematic of Component 2 X 1 MUX

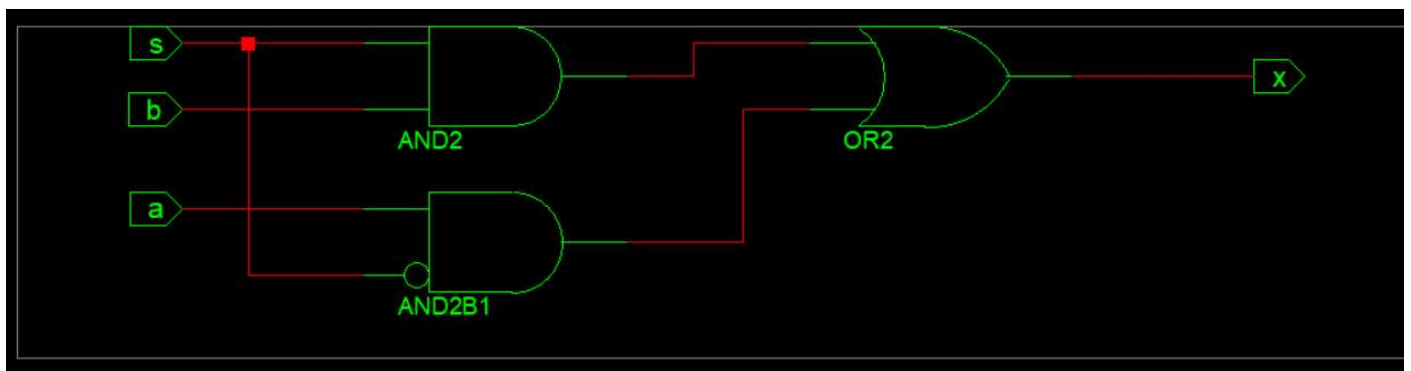

Detailed RTL Schematic of Component 2 X 1 MUX



### Technology Schematic